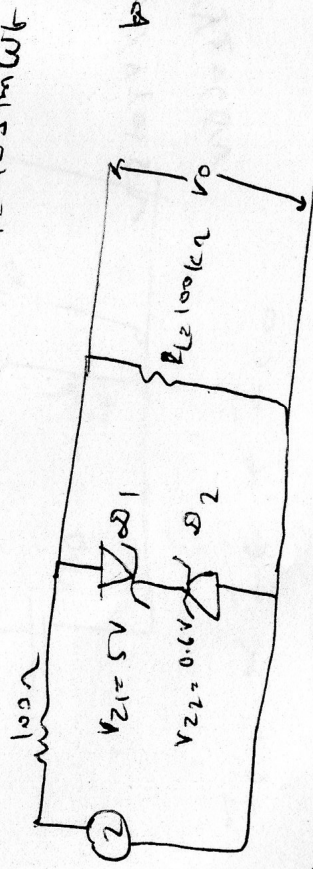


Q1 Draw the Output Voltage Waveform of the circuit given below! -

$V_i = 10 \sin \omega t$



Ans 1- $V_{O2} = \frac{10 \sin \omega t}{100.1k\Omega} \times 100k\Omega$


in the half cycle $\uparrow$

$V_i > 0.6V$ behaves as a battery

Discharge D_2 acts.

In the half cycle $V_i < 0.6V$

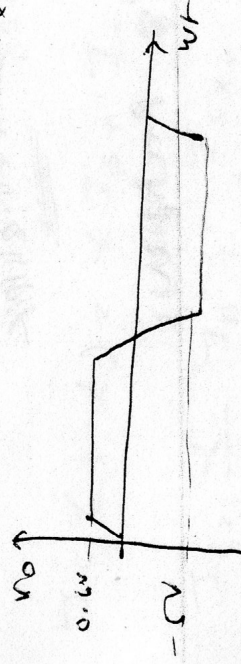$\& V_i > 5V$ behaves as battery V_{O2} follows V_{in}



OR Compare BJT with FET? (Three difference)!

Ans. BJT

① 3 terminals in BJT

(Emitter, base, collector)

FET

3 terminal

(Source, gate, drain)

② BJT is Current

Controlled device.

Voltage Controlled device.

③ Input Impedance is lower.

Input Impedance is very high

MODEL TEST PAPER

Q3. Transition Capacitance of an abrupt junction diode is 20pF at 5V. Compute the decrease in capacitance for 1V increase in bias.

Ans. $J_N C_T = \epsilon A / t$, $t \propto V^{1/2}$
 $C_T \propto V^{-1/2}$

So $C_{T1} = 20\text{pF}$, $V_1 = 5\text{V}$
 $C_{T2} = ?$, $V_2 = 6\text{V}$

$$\frac{C_{T2}}{C_{T1}} = \left(\frac{V_1}{V_2} \right)^{1/2}$$

$$C_{T2} = C_{T1} \left(\frac{V_1}{V_2} \right)^{1/2} = 20 \times 10^{-12} \times \left(\frac{5}{6} \right)^{1/2} = 18.25\text{pF}$$


Decrease in capacitance = $20 - 18.25 = 1.75\text{pF}$

Q4. Compare different type of Rectifiers.

S.N	Particular	Half wave	Centre tap	Bridge
1	No. of diodes	one	Two	four
2	maximum η	40.6%	81.2%	81.2%
3	P.T.V.	V_m	$2V_m$	V_m
4	Ripple factor	1.21	0.48	0.48

Draw the circuit diagram of CE stage of BJT & find the Relation between α and β .

Ans

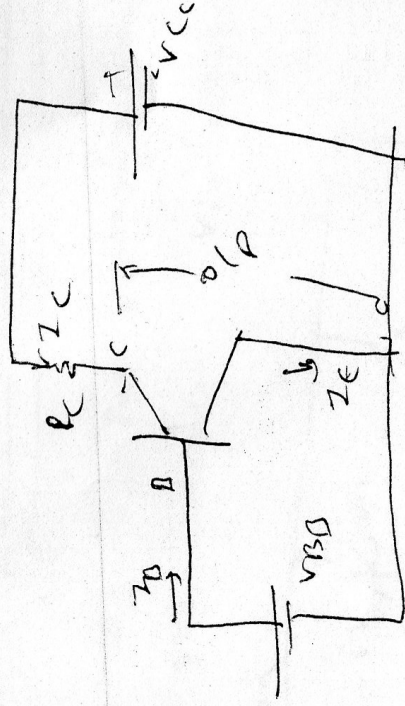

$$I_C = I_E + I_{C0}$$

$$I_{C0} \approx I_{C00}$$

$$I_C \approx I_E + I_{C00}$$

$$I_E = I_B + I_C$$

$$I_C \approx (I_B + I_C) + I_{C00}$$

$$I_C (1 - \alpha) \approx I_B + I_{C00}$$

$$I_C \approx \frac{I_B}{1 - \alpha} + \frac{I_{C00}}{1 - \alpha}$$

$$\boxed{I_C = \beta I_B + I_{C00}}$$

Relation

$$\beta = \frac{\Delta I_C}{\Delta I_B}$$

$$, \alpha = \frac{\Delta I_C}{\Delta I_E}$$

$$\beta = \frac{\Delta I_C}{\Delta I_E - \Delta I_C}$$

$$\frac{\Delta I_C}{\Delta I_E} = \frac{\Delta I_C}{1 - \frac{\Delta I_C}{\Delta I_C}}$$

$$= \frac{\alpha}{1 - \alpha}$$

$$\beta_2 \frac{\alpha}{1-\alpha}$$

$$\beta - \beta\alpha = \alpha$$

$$\beta_2 \beta\alpha = \alpha$$

$$\beta_2 \alpha (1 + \beta)$$

$$\alpha = \frac{\beta}{1 + \beta}$$

$$\beta_2 \frac{\alpha}{1-\alpha}$$

MAYANK MEWARA

Dept: Electronics & Comm Engg.

Post: Asst. Professor